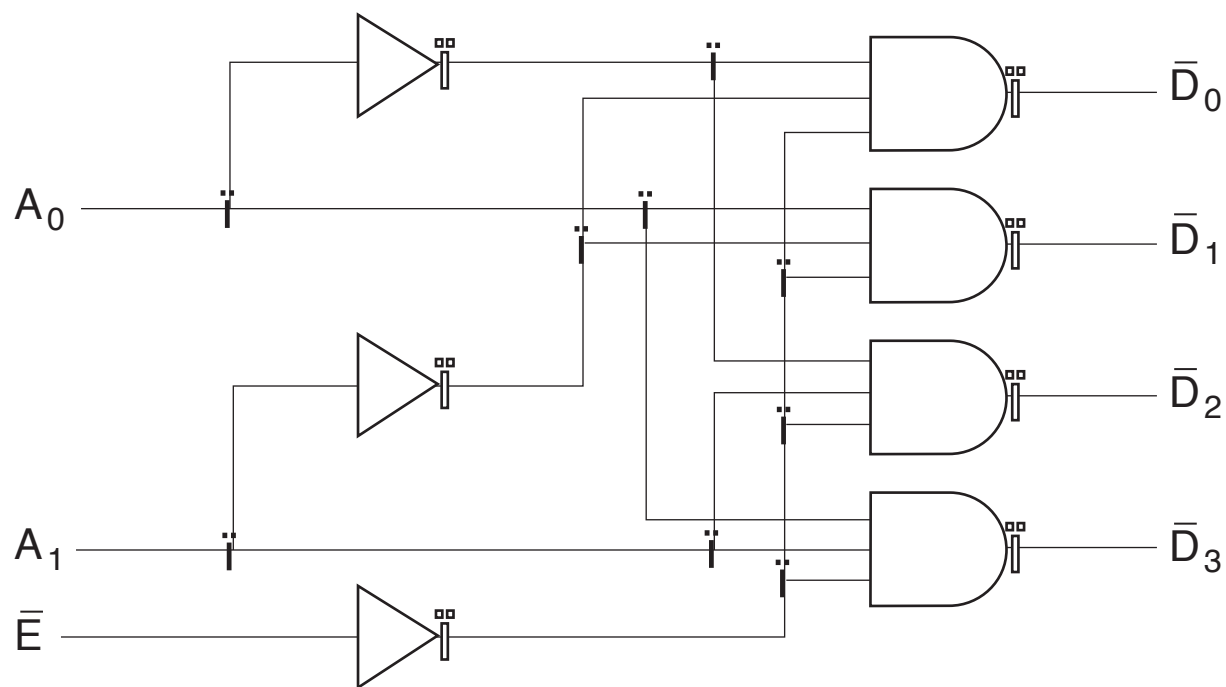


CSE-45208

Introduction to VHDL

Dr. Izadi

Figure 3-14 A 2-to-4-Line Decoder



(a) Logic diagram

| \bar{E} | A_1 | A_0 | \bar{D}_0 | \bar{D}_1 | \bar{D}_2 | \bar{D}_3 |
|-----------|-------|-------|-------------|-------------|-------------|-------------|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | X | X | 1 | 1 | 1 | 1 |

(b) Truth table

$$\bar{D}_0 = \bar{E} \bar{A}_1 \bar{A}_0$$

$$\bar{D}_1 = \bar{E} \bar{A}_1 A_0$$

$$\bar{D}_2 = \bar{E} A_1 \bar{A}_0$$

$$\bar{D}_3 = \bar{E} A_1 A_0$$

(c) Logic Equations

Figure 3-36 Structural VHDL Description of a 2-to-4 Line Decoder

```

-- 2-to-4 Line Decoder: Structural VHDL Description      -- 1
-- (See Figure 3-14 for logic diagram)                 -- 2
library ieee, lcdf_vhdl;                               -- 3
use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all; -- 4
entity decoder_2_to_4 is                               -- 5
  port(E_n, A0, A1: in std_logic;                     -- 6
        D0_n, D1_n, D2_n, D3_n: out std_logic);      -- 7
end decoder_2_to_4;                                   -- 8
-- 9
architecture structural_1 of decoder_2_to_4 is         --10
  component NOT1                                       --11
    port(in1: in std_logic;                            --12
          out1: out std_logic);                       --13
  end component;                                       --14
  component NAND3                                       --15
    port(in1, in2, in3: in std_logic;                 --16
          out1: out std_logic);                       --17
  end component;                                       --18
  signal E, A0_n, A1_n: std_logic;                    --19
begin                                                  --20
  g0: NOT1 port map (in1 => A0, out1 => A0_n);        --21
  g1: NOT1 port map (in1 => A1, out1 => A1_n);        --22
  g2: NOT1 port map (in1 => E_n, out1 => E);          --23
  g3: NAND3 port map (in1 => A0_n, in2 => A1_n,       --24
                     in3 => E, out1 => D0_n);        --25
  g4: NAND3 port map (in1 => A0, in2 => A1_n,         --26
                     in3 => E, out1 => D1_n);        --27
  g5: NAND3 port map (in1 => A0_n, in2 => A1,         --28
                     in3 => E, out1 => D2_n);        --29
  g6: NAND3 port map (in1 => A0, in2 => A1,          --30
                     in3 => E, out1 => D3_n);        --31
end structural_1;                                     --32

```

Figure 3-19 4-to-1-Line Multiplexer

 


Figure 3-37 Structural VHDL Description of a 4-to-1 Line Multiplexer

```

-- 4-to-1 Line Multiplexer: Structural VHDL Description -- 1
-- (See Figure 3-19 for logic diagram) -- 2
library ieee, lcdf_vhdl; -- 3
use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all; -- 4
entity multiplexer_4_to_1_st is -- 5
  port(S: in std_logic_vector(0 to 1); -- 6
        D: in std_logic_vector(0 to 3); -- 7
        Y: out std_logic); -- 8
end multiplexer_4_to_1_st; -- 9
--10
architecture structural_2 of multiplexer_4_to_1_st is --11
  component NOT1 --12
    port(in1: in std_logic; --13
          out1: out std_logic); --14
  end component; --15
  component AND3 --16
    port(in1, in2, in3: in std_logic; --17
          out1: out std_logic); --18
  end component; --19
  component OR4 --20
    port(in1, in2, in3, in4: in std_logic; --21
          out1: out std_logic); --22
  end component; --23
  signal S_n: std_logic_vector(0 to 1); --24
  signal N: std_logic_vector(0 to 3); --25
begin --26
  g0: NOT1 port map (S(0), S_n(0)); --27
  g1: NOT1 port map (S(1), S_n(1)); --28
  g2: AND3 port map (S_n(1), S_n(0), D(0), N(0)); --29
  g3: AND3 port map (S_n(1), S(0), D(1), N(1)); --30
  g4: AND3 port map (S(1), S_n(0), D(2), N(2)); --31
  g5: AND3 port map (S(1), S(0), D(3), N(3)); --32
  g6: OR4 port map (N(0), N(1), N(2), N(3), Y); --33
end structural_2; --34

```

```
-- 2-to-4 Line Decoder: Dataflow VHDL Description      -- 1
-- (See Figure 3-14 for logic diagram)                -- 2
Use library, use, and entity entries from 2_to_4_decoder_st;
--3

architecture dataflow_1 of decoder_2_to_4 is          -- 4

signal A0_n, A1_n: std_logic;                       -- 5
begin                                               -- 6
  A0_n <= not A0;                                   -- 7
  A1_n <= not A1;                                   -- 8
  E <= not E_n;                                     -- 9
  D0_n <= not ( A0_n and A1_n and E );              --10
  D1_n <= not ( A0_n and A1_n and E );              --11
  D2_n <= not ( A0_n and A1_n and E );              --12
  D3_n <= not ( A0_n and A1_n and E );              --13
  D3_n <= not ( A0_n and A1_n and E );              --14
  D3_n <= not ( A0_n and A1_n and E );              --15
```

3-48 Figure 3-39 Conditional Dataflow VHDL Description of a 4-to-1 Line Multiplexer Using When-Else

```
-- 4-to-1 Line Mux: Conditional Dataflow VHDL Description--1
-- Using When-Else (See Figure 3-19 for function table) -- 2
library ieee; -- 3
use ieee.std_logic_1164.all; -- 4
entity multiplexer_4_to_1_we is -- 5
    port (S : in std_logic_vector(1 downto 0); -- 6
          D : in std_logic_vector(0 to 3); -- 7
          Y : out std_logic); -- 8
end multiplexer_4_to_1_we; -- 9
--10
architecture function_table of multiplexer_4_to_1_we is --11
begin --12
    Y <=D(0) when S = "00" else --13
        D(1) when S = "01" else --14
        D(2) when S = "10" else --15
        D(3) when S = "11" else --16
        'X'; --17
end function_table; --18
```

3-49 Figure 3-40 Conditional Dataflow VHDL Description of a 4-to-1 Line Multiplexer Using With-Select

```
--4-to-1 Line Mux: Conditional Dataflow VHDL Description-- 1
Using When-Else (See Figure 3-14 for logic equations) -- 2
library ieee; -- 3
use ieee.std_logic_1164.all; -- 4
entity multiplexer_4_to_1_ws is -- 5
    port (S : in std_logic_vector(1 downto 0); -- 6
          D : in std_logic_vector(0 to 3); -- 7
          Y : out std_logic); -- 8
end multiplexer_4_to_1_ws; -- 9
--10
architecture function_table_ws of multiplexer_4_to_1_ws is--
11
begin --12
    with S select --13
        Y <=D(0) when "00", --14
          D(1) when "01", --15
          D(2) when "10", --16
          D(3) when "11", --17
          'X' when others; --18
```


Figure 3-41 Hierarchical Structural/Dataflow Description of a 4-Bit Adder

```

-- 4-bit Adder: Hierarchical Dataflow/Structural
-- (See Figures 3-27 and 3-28 for logic diagrams)
library ieee;
use ieee.std_logic_1164.all;
entity half_adder is
    port (x, y : in std_logic;
          s, c : out std_logic);
end half_adder;

architecture dataflow_3 of half_adder is
begin
    s <= x xor y;
    c <= x and y;
end dataflow_3;

library ieee;
use ieee.std_logic_1164.all;
entity full_adder is
    port (x, y, z : in std_logic;
          s, c : out std_logic);
end full_adder;

architecture struc_dataflow_3 of full_adder is
    component half_adder
        port(x, y : in std_logic;
             s, c : out std_logic);
    end component;
    signal hs, hc, tc: std_logic;
begin
    HA1: half_adder
        port map (x, y, hs, hc);
    HA2: half_adder
        port map (hs, z, s, tc);
    c <= tc or hc;
end struc_dataflow_3;

library ieee;
use ieee.std_logic_1164.all;
entity adder_4 is
    port(B, A : in std_logic_vector(3 downto 0);
          C0 : in std_logic;
          S : out std_logic_vector(3 downto 0);
          C4: out std_logic);
end adder_4;

```

```
architecture structural_4 of adder_4 is
  component full_adder
    port(x, y, z : in std_logic;
         s, c : out std_logic);
  end component;
  signal C: std_logic_vector(4 downto 0);
begin
  Bit0: full_adder
    port map (B(0), A(0), C(0), S(0), C(1));
  Bit1: full_adder
    port map (B(1), A(1), C(1), S(1), C(2));
  Bit2: full_adder
    port map (B(2), A(2), C(2), S(2), C(3));
  Bit3: full_adder
    port map (B(3), A(3), C(3), S(3), C(4));
  C(0) <= C0;
  C4 <= C(4);
end structural_4;
```

Figure 3-43 Behavioral Description of a 4-Bit Adder

```
architecture structural_4 of adder_4 is
  component full_adder
    port(x, y, z : in std_logic;
         s, c : out std_logic);
  end component;
  signal C: std_logic_vector(4 downto 0);
begin
  Bit0: full_adder
    port map (B(0), A(0), C(0), S(0), C(1));
  Bit1: full_adder
    port map (B(1), A(1), C(1), S(1), C(2));
  Bit2: full_adder
    port map (B(2), A(2), C(2), S(2), C(3));
  Bit3: full_adder
    port map (B(3), A(3), C(3), S(3), C(4));
  C(0) <= C(0);
  C4 <= C(4);
end structural_4;
```