

STATE UNIVERSITY OF NEW YORK  
New Paltz, New York.

General Physics 2  
Second Exam

Instructor: Dr. T. Biswas  
April 8, 2024.

# Solutions

## Constants and Formulas

$$\mu_0 = 4\pi \times 10^{-7} \text{ Tm/A.}$$

$$V = iR$$

$$q = CV$$

$$C = C_1 + C_2$$


$$1/C = 1/C_1 + 1/C_2$$

$$\vec{\mathbf{F}} = i\vec{\mathbf{L}} \times \vec{\mathbf{B}}$$

$$\begin{aligned} d\vec{\mathbf{B}} &= \frac{\mu_0 i}{4\pi r^2} d\vec{\mathbf{S}} \times \hat{\mathbf{r}} \\ &= \frac{\mu_0 i}{4\pi r^3} d\vec{\mathbf{S}} \times \vec{\mathbf{r}} \end{aligned}$$

Name \_\_\_\_\_

## Problem I

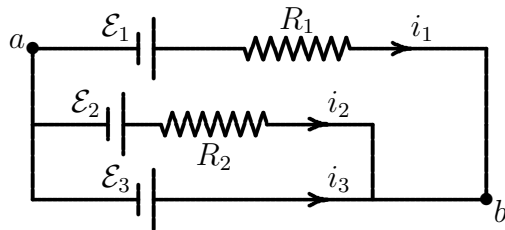

The above circuit has components of the following values:  $R_1 = 4.0 \Omega$ ,  $R_2 = 8.0 \Omega$ ,  $\mathcal{E}_1 = 20 \text{ V}$ ,  $\mathcal{E}_2 = 30 \text{ V}$ , and  $\mathcal{E}_3 = 50 \text{ V}$ . Consider the current directions as shown.

## Solution

### Question 1

The outer rectangular loop gives

$$\mathcal{E}_1 - i_1 R_1 - \mathcal{E}_3 = 0.$$

Hence,

$$i_1 = \frac{\mathcal{E}_1 - \mathcal{E}_3}{R_1} = -7.5 \text{ A}$$

### Question 2

The lower rectangular loop gives

$$\mathcal{E}_2 - i_2 R_2 - \mathcal{E}_3 = 0.$$

Hence,

$$i_2 = \frac{\mathcal{E}_2 - \mathcal{E}_3}{R_2} = -2.5 \text{ A}$$

### Question 3

The junction equation gives

$$i_1 + i_2 + i_3 = 0$$

Hence,

$$i_3 = -i_2 - i_1 = 10 \text{ A}$$

### Question 4


Starting at  $a$ , going down and then going right along the bottom branch to  $b$  encounters the source  $\mathcal{E}_3$ . Hence,

$$V_a + \mathcal{E}_3 = V_b$$

Hence,

$$V_b - V_a = \mathcal{E}_3 = 50 \text{ V}$$

## Problem II

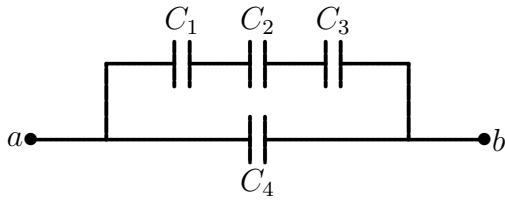

Four capacitors are connected as shown above. Each capacitor has a capacitance of  $6.0\mu\text{F}$ . A voltage of  $10\text{V}$  is applied between the points  $a$  and  $b$ .

## Solution

### Question 5

$C_1$ ,  $C_2$  and  $C_3$  are in series. So their combination has capacitance  $C_s$  given by

$$1/C_s = 1/C_1 + 1/C_2 + 1/C_3 = 1/2$$

Hence,

$$C_s = 2.0$$

$C_s$  and  $C_4$  are in parallel. Hence, the net capacitance  $C$  is given by

$$C = C_s + C_4 = 8.0\mu\text{F}$$

### Question 6

The full voltage of  $10\text{V}$  is across the capacitance  $C_s$ . The charge in the series combination is the same as the charge in each member of the combination. Hence,


$$q_1 = q_s = C_s V = 2.0 \times 10 = 20\mu\text{C}$$

### Question 7

The voltage across  $C_4$  is  $10\text{V}$ . Hence the charge in it is

$$q_4 = C_4 V = 6.0 \times 10 = 60\mu\text{C}.$$

### Problem III

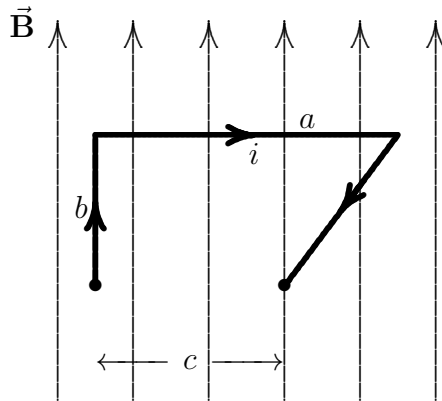

The figure above shows a magnetic field  $\vec{B}$  directed towards the top of the page. Its magnitude is 2.0T. A piece of wire is placed in this magnetic field in the plane of the page as shown. The top segment has a length  $a = 4.0\text{m}$  and the left segment has a length  $b = 2.0\text{m}$ . The distance between the ends of the wire is  $c = 2.5\text{m}$ . A current of  $i = 5.0\text{A}$  is flowing in the wire in the direction shown.

### Solution

#### Question 8

The force is given by

$$\vec{F} = i\vec{L} \times \vec{B}$$

The right hand rule gives the direction of  $\vec{F}$  to be out of the page. The magnitude is

$$F = i|\vec{L} \times \vec{B}| = iaB \sin 90^\circ = 40 \text{ N}$$

#### Question 9

The magnitude is


$$F = i|\vec{L} \times \vec{B}| = ibB \sin 0^\circ = 0 \text{ N}$$

#### Question 10

Here, the vector  $\vec{L}$  is the one joining the end-points in the direction of the current. So, the right hand rule gives the direction of  $\vec{F}$  to be out of the page. The magnitude is

$$F = i|\vec{L} \times \vec{B}| = icB \sin 90^\circ = 25 \text{ N}$$

## Problem IV

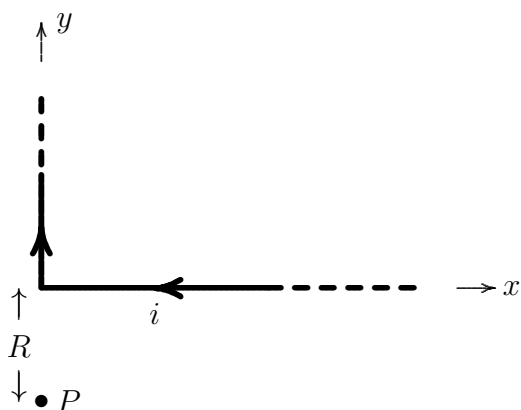


A long thin wire is bent in the shape shown above. Assume it extends to infinity in the positive  $y$  and positive  $x$  directions as shown. A current  $i$  flows in the wire as shown. The point marked  $P$  is at a distance  $R$  along the negative  $y$  axis as shown.

## Solution

Biot-Savart law gives

$$d\vec{B} = \frac{\mu_0 i}{4\pi r^2} d\vec{s} \times \hat{r}$$

## Question 11

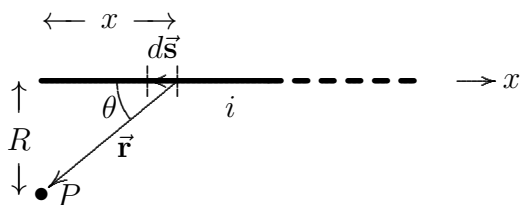

Using the right-hand-rule, the magnetic field direction due to the element of wire  $d\vec{s}$  is found to be out of the page. As this direction is the same for all elements of wire, in-

tegrating the magnitude of the field will give the total field.

$$dB = \frac{\mu_0 i}{4\pi r^2} ds \sin \theta$$

where  $\sin \theta = R/r$ . Hence,

$$B = \int dB = \frac{\mu_0 i R}{4\pi} \int \frac{ds}{r^3}$$

Choosing the left end of the wire as the origin of the  $x$  axis and the distance of the line element from the origin to be  $x$ , it follows that  $ds = dx$  and  $r = (x^2 + R^2)^{1/2}$ . Hence,

$$B = \frac{\mu_0 i R}{4\pi} \int_0^\infty \frac{dx}{(x^2 + R^2)^{3/2}}$$

## Question 12

For this part, the angle between  $d\vec{s}$  and  $\hat{r}$  is zero. So,  $d\vec{s} \times \hat{r} = 0$ . Hence, the magnetic field due to this part is zero.

## Question 13

Direction is out of the page as seen in the solution of question 11.

Name \_\_\_\_\_

**1** a b c d e f g h i j

**2** a b c d e f g h i j

**3** a b c d e f g h i j

**4** a b c d e f g h i j

**5** a b c d e f g h i j

**6** a b c d e f g h i j

**7** a b c d e f g h i j

**8** a b c d e f g h i j

**9** a b c d e f g h i j

**10** a b c d e f g h i j

**11** a b c d e f g h i j

**12** a b c d e f g h i j

**13** a b c d e f g h i j

**14** a b c d e f g h i j

**15** a b c d e f g h i j

**16** a b c d e f g h i j

**17** a b c d e f g h i j

**18** a b c d e f g h i j

**19** a b c d e f g h i j

**20** a b c d e f g h i j